

## **VHDL LAB #6**

Rachel Ruddy - 261162987

Natasha Lawford - 261178596

Rachel Bunsick - 261159677

### **I. Executive Summary:**

In this lab, we created a sequence detector to detect the instance of the 4-bit patterns “0010” and “1011” from a given input sequence of 1 bit numbers. The sequence detector utilizes two FSMs, one to detect the former pattern and one to detect the latter pattern. In the next part, we combined the logic of the sequence detector with a counter to keep track of the number of times that a given sequence occurred following each instance. Finally, we used the clock divider we created in Lab #5 to read and count the sequence from a ROM file by reading one bit every one second.

## Sequence Detector Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity rachel_ruddy_FSM is
6  port (seq : in std_logic;
7        enable : in std_logic;
8        reset : in std_logic;
9        clk : in std_logic;
10       out_1 : out std_logic;
11       out_2 : out std_logic);
12 end rachel_ruddy_FSM;
13
14 architecture behavioral of rachel_ruddy_FSM is
15
16     -- States for FSM detecting "1011"
17     type fsm1_state_type is (S0, S1, S2, S3, S4);
18     signal fsm1_state, fsm1_next_state : fsm1_state_type;
19
20     -- States for FSM detecting "0010"
21     type fsm2_state_type is (T0, T1, T2, T3, T4);
22     signal fsm2_state, fsm2_next_state : fsm2_state_type;
23
24 begin
25     process(clk, reset)
26     begin
27         if reset = '1' then
28             fsm1_state <= S0;
29             fsm2_state <= T0;
30         elsif rising_edge(clk) then
31             if enable = '1' then
32                 fsm1_state <= fsm1_next_state;
33                 fsm2_state <= fsm2_next_state;
34             else
35                 fsm1_state <= fsm1_state;
36                 fsm2_state <= fsm2_state;
37             end if;
38         end if;
39     end process;
40
41     -- FSM 1 Behavior
42     process (fsm1_state, seq)
43     begin
44         out_1 <= '0';
45         case fsm1_state is
46             when S0 =>
47                 if seq = '1' then
48                     fsm1_next_state <= S1;
49                 else
50                     fsm1_next_state <= S0;
```

```

51         end if;
52     when S1 =>
53         if seq = '0' then
54             fsm1_next_state <= S2;
55         else
56             fsm1_next_state <= S1;
57         end if;
58     when S2 =>
59         if seq = '1' then
60             fsm1_next_state <= S3;
61         else
62             fsm1_next_state <= S0;
63         end if;
64     when S3 =>
65         if seq = '1' then
66             fsm1_next_state <= S4;
67         else
68             fsm1_next_state <= S2;
69         end if;
70     when S4 =>
71         if seq = '1' then
72             fsm1_next_state <= S1;
73             out_1 <= '1';
74         else
75             fsm1_next_state <= S2;
76             out_1 <= '1';
77         end if;
78     when others =>
79         fsm1_next_state <= S0;
80     end case;
81 end process;
82
83 -- FSM 2 Behavior
84 process (fsm2_state, seq)
85 begin
86     out_2 <= '0';
87     case fsm2_state is
88     when T0 =>
89         if seq = '0' then
90             fsm2_next_state <= T1;
91         else
92             fsm2_next_state <= T0;
93         end if;
94     when T1 =>
95         if seq = '0' then
96             fsm2_next_state <= T2;
97         else
98             fsm2_next_state <= T0;
99         end if;
100     when T2 =>
101         if seq = '1' then
102             fsm2_next_state <= T3;
103         else
104             fsm2_next_state <= T2;
105         end if;
106     when T3 =>
107         if seq = '0' then
108             fsm2_next_state <= T4;
109         else
110             fsm2_next_state <= T1;
111         end if;
112     when T4 =>
113         if seq = '1' then
114             fsm2_next_state <= T0;
115             out_2 <= '1';
116         else
117             fsm2_next_state <= T2;
118             out_2 <= '1';
119         end if;
120     when others =>
121         fsm2_next_state <= T0;
122     end case;
123 end process;
124
125 end behavioral;

```

The sequence detector code defines a new type of variables of state type to represent each of the five states for our two FSMs. First, we create a clock process which is triggered at the change of the clock input or reset input. We hand the reset case and additionally change the state of the FSM on the rising edge of the clock. Then, based on the state diagrams attached below the testbench, the logic for the state transitions along with the output is used in a process which is triggered when the state is changed.

### Sequence Detector Testbench:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity FSM_tb is
6  | end FSM_tb;
7
8  architecture behavioral of FSM_tb is
9  |
10 |     component rachel_ruddy_FSM
11 |     | Port (seq      : in std_logic;
12 |           enable    : in std_logic;
13 |           reset     : in std_logic;
14 |           clk       : in std_logic;
15 |           out_1     : out std_logic;
16 |           out_2     : out std_logic);
17 |     end component;
18
19 |     signal seq_tb : std_logic := '0';
20 |     signal enable_tb : std_logic := '0';
21 |     signal reset_tb : std_logic := '0';
22 |     signal clk_tb : std_logic := '0';
23 |     signal out_1tb : std_logic := '0';
24 |     signal out_2tb : std_logic := '0';
25
26 |     constant clk_period : time := 10 ns;
27
28 |     begin
29
30 |     uut: rachel_ruddy_FSM
31 |     | port map (
32 |         seq => seq_tb,
33 |         enable => enable_tb,
34 |         reset => reset_tb,
35 |         clk => clk_tb,
36 |         out_1 => out_1tb,
37 |         out_2 => out_2tb
38 |     );
39
40 |     clk_process: process
41 |     | begin
42 |     |     while true loop
43 |     |         clk_tb <= '0';
44 |     |         wait for clk_period / 2;
45 |     |         clk_tb <= '1';
46 |     |         wait for clk_period / 2;
47 |     |     end loop;
48 |     end process;
49

```

```
50 stimulus_process: process
51 begin
52
53 -- initialize
54 reset_tb <= '0';
55 wait for clk_period * 2;
56
57 reset_tb <= '1';
58 wait for clk_period * 2;
59
60 -- enable FSM
61 enable_tb <= '1';
62 wait for clk_period * 2;
63
64 seq_tb <= '0';
65 wait for clk_period * 2;
66
67 seq_tb <= '0';
68 wait for clk_period * 2;
69
70 seq_tb <= '1';
71 wait for clk_period * 2;
72
73 seq_tb <= '0';
74 wait for clk_period * 2;
75
76 seq_tb <= '1';
77 wait for clk_period * 2;
78
79 seq_tb <= '1';
80 wait for clk_period * 2;
81
82 seq_tb <= '0';
83 wait for clk_period * 2;
84
85 seq_tb <= '1';
86 wait for clk_period * 2;
87
88 seq_tb <= '0';
89 wait for clk_period * 2;
90
91 seq_tb <= '1';
92 wait for clk_period * 2;
93
94 seq_tb <= '1';
95 wait for clk_period * 2;
96
97 seq tb <= '0':
```

```



97     seq_tb <= '0';
98     wait for clk_period * 2;
99
100    seq_tb <= '1';
101    wait for clk_period * 2;
102
103    seq_tb <= '1';
104    wait for clk_period * 2;
105
106    seq_tb <= '0';
107    wait for clk_period * 2;
108
109    -- try reset
110    reset_tb <= '1';
111    wait for clk_period * 2;
112
113    seq_tb <= '0';
114    wait for clk_period * 2;
115
116    seq_tb <= '0';
117    wait for clk_period * 2;
118
119    seq_tb <= '1';
120    wait for clk_period * 2;
121
122    seq_tb <= '0';
123    wait for clk_period * 2;
124
125    seq_tb <= '0';
126    wait for clk_period * 2;
127
128    wait for clk_period * 20;
129
130    wait;
131    end process;
132
133 end behavioral;
134

```

The sequence detector testbench tests exhaustively the functionality of the detector by feeding it a specific input sequence to confirm that each state transition occurs as expected and that the expected output matches the functionality. Additionally, the reset and enable functions are tested to ensure that the behavior is what we expect.

## State Diagrams for FSMs:

State Diagram:

 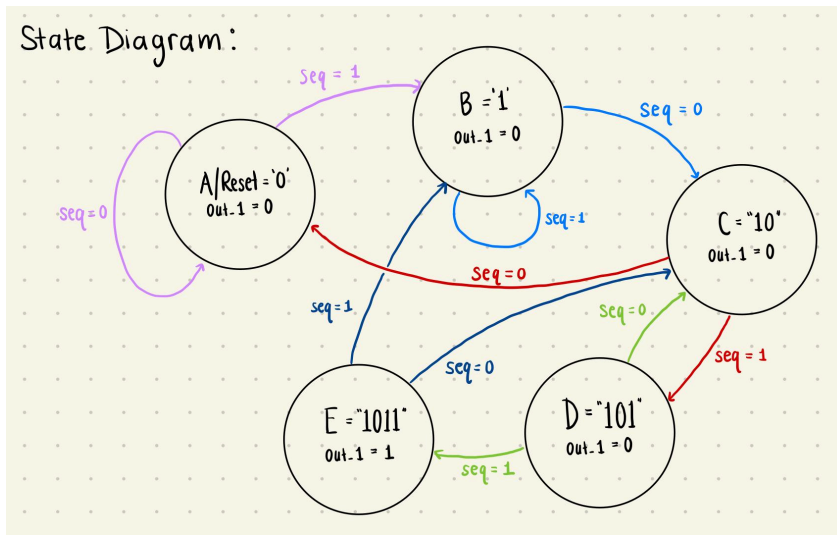

Above are the state diagrams for each sequence.

## Sequence counter:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity rachel_ruddy_sequence_detector is
6  port (seq : in std_logic;
7        enable: in std_logic;
8        reset : in std_logic;
9        clk : in std_logic;
10       cnt_1 : out std_logic_vector(2 downto 0); -- Count for "1011"
11       cnt_2 : out std_logic_vector(2 downto 0) -- Count for "0010"
12       );
13  end rachel_ruddy_sequence_detector;
14
15  Architecture Behavioral of rachel_ruddy_sequence_detector is
16  component rachel_ruddy_FSM is
17  port (seq : in std_logic;
18        enable : in std_logic;
19        reset : in std_logic;
20        clk : in std_logic;
21        out_1 : out std_logic;
22        out_2 : out std_logic);
23  end component;
24
25  signal out_1, out_2: std_logic := '0';
26  signal count_1, count_2: unsigned(2 downto 0) := "000";
27
28  begin
29
30  FSM_inst: rachel_ruddy_FSM -- instantiate the sequence detector
31  port map (seq => seq,
32            enable => enable,
33            reset => reset,
34            clk => clk,
35            out_1 => out_1,
36            out_2 => out_2
37            );
38
39  Process (clk, reset)
40  begin
41  If reset = '0' then --overrides everything:
42  count_2 <= "000"; --reset both counts to 0
43  count_1 <= "000";
44  elsif rising_edge(clk) then -- if not reset, then check to see what happens on rising edge
45
46  If enable = '1' then --if enable is on and sequence detected, add 1 to count(s)
47  if out_1 = '1' then
48  count_1 <= count_1 + 1;
49  end if;
50  If out_2 = '1' then
51  count_2 <= count_2 + 1;
52  end if;
53  end if;
54  end if;
55  end process;
56
57  cnt_1 <= std_logic_vector(count_1);
58  cnt_2 <= std_logic_vector(count_2);
59
60  end Behavioral;
61
```

The sequence counter instantiates the FSM to detect the two given sequences from an output bit, but it additionally keeps track of the number of times that each output for the sequences has been 1.



### Sequence counter testbench:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity counter_tb is
6  end counter_tb;
7
8  architecture behavioral of counter_tb is
9  |
10 |     component rachel_ruddy_sequence_detector
11 |     port (seq      : in std_logic;
12 |           enable   : in std_logic;
13 |           reset    : in std_logic;
14 |           clk      : in std_logic;
15 |           cnt_1    : out std_logic;
16 |           cnt_2    : out std_logic);
17 |     end component;
18 |
19 |     signal seq_tb : std_logic := '0';
20 |     signal enable_tb : std_logic := '0';
21 |     signal reset_tb : std_logic := '0';
22 |     signal clk_tb : std_logic := '0';
23 |     signal cnt_1tb : std_logic := '0';
24 |     signal cnt_2tb : std_logic := '0';
25 |
26 |     constant clk_period : time := 10 ns;
27 |
28 |     begin
29 |
30 |     uut: rachel_ruddy_sequence_detector
31 |     port map (
32 |         seq => seq_tb,
33 |         enable => enable_tb,
34 |         reset => reset_tb,
35 |         clk => clk_tb,
36 |         cnt_1 => cnt_1tb,
37 |         out_2 => cnt_2tb
38 |     );
39 |
40 |     clk_process: process
41 |     begin
42 |         while true loop
43 |             clk_tb <= '0';
44 |             wait for clk_period / 2;
45 |             clk_tb <= '1';
46 |             wait for clk_period / 2;
47 |         end loop;
48 |     end process;
49 |
50 |     stimulus_process: process
51 |     begin
52 |
53 |         -- initialize
```

```

54     reset_tb <= '1';
55     wait for clk_period * 2;
56
57     report "Starting stimulus process" severity note;
58     reset_tb <= '0';
59     wait for clk_period * 2;
60
61
62     reset_tb <= '1';
63     wait for clk_period * 2;
64
65     -- enable FSM
66     enable_tb <= '1';
67     wait for clk_period * 2;
68
69     -- sequence: 1011001001010
70     -- cnt1 : 1011
71     -- cnt2 : 0010
72     seq_tb <= '1';
73     wait for clk_period * 2;
74
75     seq_tb <= '0';
76     wait for clk_period * 2;
77
78     seq_tb <= '1';
79     wait for clk_period * 2;
80
81     seq_tb <= '1'; -- sequence 1 detected- cnt_1 = 001
82     wait for clk_period * 2;
83
84     seq_tb <= '0';
85     wait for clk_period * 2;
86
87     seq_tb <= '0';
88     wait for clk_period * 2;
89
90     seq_tb <= '1';
91     wait for clk_period * 2;
92
93     seq_tb <= '0';
94     wait for clk_period * 2; -- sequence 2 detected- cnt_2 = 001
95
96     seq_tb <= '0';
97     wait for clk_period * 2;
98
99     seq_tb <= '1';
100    wait for clk_period * 2;
101
102    seq_tb <= '0'; -- sequence 2 detected again - cnt_2 = 010
103    wait for clk_period * 2;
104
105    --reset test! cnt_1 = 0, cnt_2 = 0

```

```

105      --reset test! cnt_1 = 0, cnt_2 = 0
106
107      reset_tb <= '0';
108      wait for clk_period * 2;
109
110      reset_tb <= '1';
111      wait for clk_period * 2;
112      -- finished reset test
113
114      -- Last sequence: 001011011
115
116      seq_tb <= '0';
117      wait for clk_period * 2;
118
119      seq_tb <= '0';
120      wait for clk_period * 2;
121
122      seq_tb <= '1';
123      wait for clk_period * 2;
124
125      seq_tb <= '0';
126      wait for clk_period * 2; -- sequence 2 detected cnt_2 = 001
127
128      seq_tb <= '1';
129      wait for clk_period * 2;
130
131      seq_tb <= '1';
132      wait for clk_period * 2; -- sequence 1 detected cnt_1 = 001
133
134      seq_tb <= '0';
135      wait for clk_period * 2;
136
137      seq_tb <= '1';
138      wait for clk_period * 2;
139
140      seq_tb <= '1';
141      wait for clk_period * 2; -- sequence 1 detected cnt_1 = 010
142
143      wait for clk_period * 20;
144      wait;
145      end process;
146
147  end behavioral;
148

```

The sequence counter testbench iterates through different edge cases to observe the behavior of the sequence detector depending on the reset and enable. The same sequence of input bits is used from the sequence detector testbench, however we are also able to check to see whether the counter is functioning as expected.

## Wrapper Code:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity rachel_ruddy_wrapper is
6  port (reset : in std_logic;
7        clk   : in std_logic;
8        HEX0  : out std_logic_vector(6 downto 0);
9        HEX5  : out std_logic_vector(6 downto 0));
10 end rachel_ruddy_wrapper;
11
12 architecture behavior of rachel_ruddy_wrapper is
13
14     component ROM is
15     port(
16         clk : in std_logic;
17         reset : in std_logic;
18         data : out std_logic);
19     end component;
20
21
22     component seven_segment_decoder is
23     port (code : in std_logic_vector (3 downto 0);
24           segments_out: out std_logic_vector(6 downto 0));
25     end component;
26
27
28     component rachel_ruddy_sequence_detector is
29     port (seq : in std_logic;
30           enable: in std_logic;
31           reset : in std_logic;
32           clk : in std_logic;
33           cnt_1 : out std_logic_vector(2 downto 0); -- Count for "1011"
34           cnt_2 : out std_logic_vector(2 downto 0) -- Count for "0010"
35           );
36     end component;
37
38
39     component rachel_ruddy_clock_divider is
40     port (enable : in std_logic;
41           reset : in std_logic;
42           clk : in std_logic;
43           en_out : out std_logic);
44     end component;
45
46     signal enable : std_logic := '1';
47     signal clk2 : std_logic := '0';
48     signal data : std_logic := '0';
49     signal cnt_1 : std_logic_vector(2 downto 0);
```

```

50 signal cnt_2 : std_logic_vector(2 downto 0);
51 signal u_cnt_1 : unsigned(3 downto 0);
52 signal u_cnt_2 : unsigned(3 downto 0);
53 signal new_cnt_1 : std_logic_vector(3 downto 0) := "0000";
54 signal new_cnt_2 : std_logic_vector(3 downto 0) := "0000";
55 signal decoded_cnt1 : std_logic_vector(6 downto 0);
56 signal decoded_cnt2 : std_logic_vector(6 downto 0);
57
58 begin
59
60 i1: rachel_ruddy_clock_divider port map (enable, reset, clk, clk2);
61 i2: ROM port map (clk2, reset, data);
62 i3: rachel_ruddy_sequence_detector port map (data, enable, reset, clk2, cnt_1, cnt_2);
63
64 u_cnt_1 <= '0' & unsigned(cnt_1);
65 new_cnt_1 <= std_logic_vector(u_cnt_1);
66 u_cnt_2 <= '0' & unsigned(cnt_2);
67 new_cnt_2 <= std_logic_vector(u_cnt_2);
68
69 i4: seven_segment_decoder port map (new_cnt_1, decoded_cnt1);
70 i5: seven_segment_decoder port map (new_cnt_2, decoded_cnt2);
71
72 HEX0 <= decoded_cnt1;
73 HEX5 <= decoded_cnt2;
74
75 end behavior;
76

```

The wrapper code instantiates the clock divider from Lab #5 and the output is used as the clock for both the ROM instance and the sequence detector instance. The sequence detector reads the output of the ROM as its input and detects the given sequences. Then, the count of the number of occurrences is mapped to 2 different seven-segment decoders so that they can be displayed on the board.

## Wrapper Testbench:

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity wrapper_tb is
6  end wrapper_tb;
7
8  architecture behavioral of wrapper_tb is
9
10     component rachel_ruddy_wrapper is
11     port (reset      : in std_logic;
12          clk         : in std_logic;
13          HEX0        : out std_logic_vector(6 downto 0);
14          HEX5        : out std_logic_vector(6 downto 0));
15     end component;
16
17     signal reset_tb : std_logic := '0';
18     signal clk_tb   : std_logic := '0';
19     signal HEX0_tb  : std_logic_vector(6 downto 0);
20     signal HEX5_tb  : std_logic_vector(6 downto 0);
21
22     constant clk_period : time := 10 ns;
23
24     begin
25
26     uut: rachel_ruddy_wrapper
27     port map (
28         reset => reset_tb,
29         clk   => clk_tb,
30         HEX0  => HEX0_tb,
31         HEX5  => HEX5_tb
32     );
33
34     clk_process: process
35     begin
36         while true loop
37             clk_tb <= '0';
38             wait for clk_period / 2;
39             clk_tb <= '1';
40             wait for clk_period / 2;
41         end loop;
42     end process;
43
44     stimulus_process: process
45     begin
46
47         reset_tb <= '0';
48         wait until rising_edge(clk_tb);
49
50         reset_tb <= '1';
51         wait until rising_edge(clk_tb);
52
53         wait for 300 sec;
54
55         wait;
56
57     end process;
58
59 end behavioral;
```

The wrapper testbench allows the wrapper instance to run for 300 seconds to observe its behavior as the data from the ROM file is read.

## II. Questions:

1. Why is it better to use two FSMs, rather than one, in the implementation of the sequence detector from Section 4?


If we were to use only one FSM to detect both sequences, it would be extremely difficult to determine different state transitions since we only have one input variable, and since the sequences are not the same, receiving 1 vs 0 will lead to conflicting states.

**2. Report the number of pins and logic modules used to fit your design on the FPGA board**

Flow Status	Successful - Mon Dec 09 16:30:51 2024
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	rachelLab6
Top-level Entity Name	rachel_ruddy_wrapper
Family	Cyclone V
Device	5CSEMA5F31C6
Timing Models	Final
Logic utilization (in ALMs)	51 / 32,070 ( < 1 % )
Total registers	51
Total pins	16 / 457 ( 4 % )
Total virtual pins	0
Total block memory bits	0 / 4,065,280 ( 0 % )
Total DSP Blocks	0 / 87 ( 0 % )
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 6 ( 0 % )
Total DLLs	0 / 4 ( 0 % )

**III. Schematics and simulation results (and explanations/labels of figures/important points on the simulation plots)**

**Sequence Detector Waveform:**

 

#### IV. Conclusions:

This lab introduced us to the concept of incorporating FSMs to create circuits which have both combinational and sequential elements. When approaching a more complex problem like this, it is important to make sure that you understand the logic and state transitions before implementation to reduce the amount of time spent debugging. Additionally, it is important to consider the efficiency of how you set up each FSM to reduce the complexity of your design.